

Name: Andrew Key

BME153L.02 (Palmeri)

Spring 2009

Test #2: Dynamic Circuit Elements and Filters

Instructions:



- Write your name at the top of each page.
- Show all work (this is *critical* for partial credit!).
- Represent all time-domain functions as such; do not leave answers in phasor notation.
- Only work in the space provided. Ask for extra paper if necessary.
- Read through each complete question before starting to work (this may save you some time).
- Remember to include units with all answers and label all plot axes.
- Clearly box all answers.

In keeping with the Duke Community Standard, I have neither given nor received aid in completion of this examination.

Signature: Andrew Key

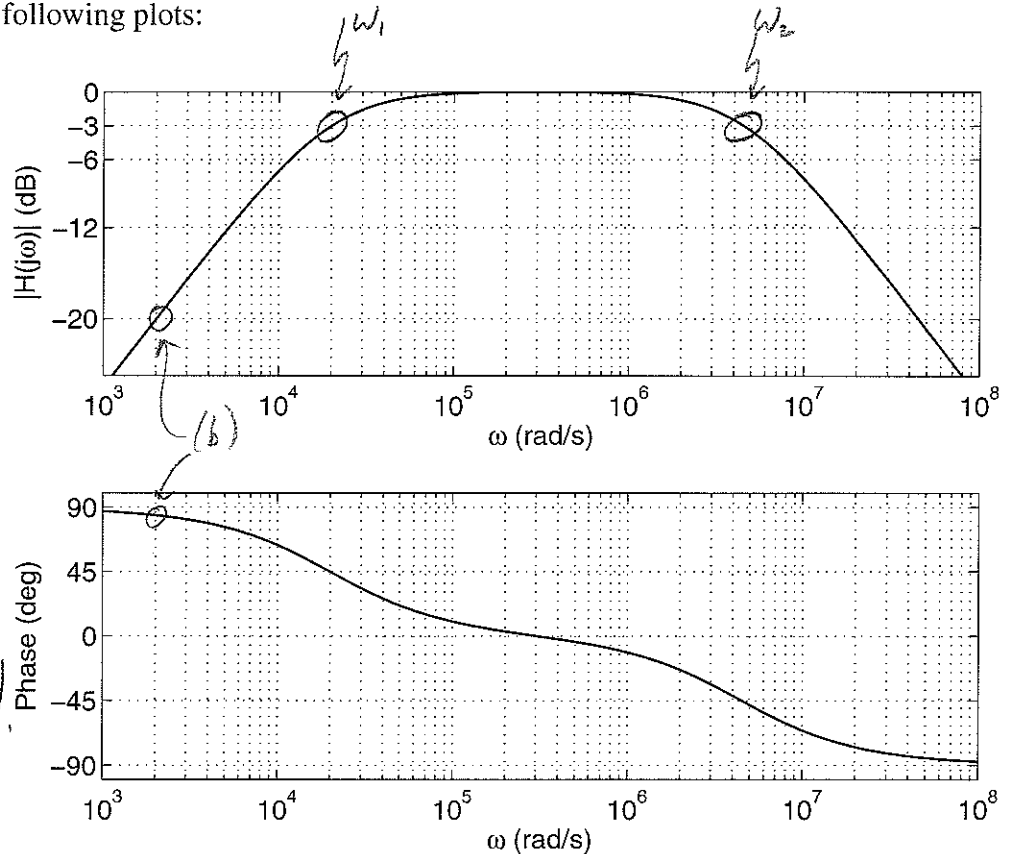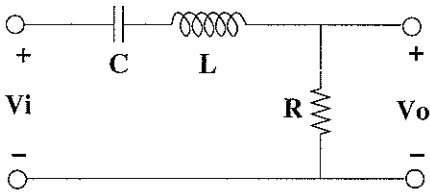Problem #1 [20 points] $\left(\frac{15.4}{20}\right)$

You're given the following filter, and you measure the magnitude and phase of its transfer function ($H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$) in the lab, as shown in the following plots:



Code used to generate these plots attached.

- (a) What type of filter is this (specify whether it is first- or second-order)? What is/are this filter's cutoff frequency/frequencies (reasonable estimates are okay)? [5 points]

BPF (2^o)

$$\left. \begin{aligned} \omega_1 &\approx 2 \times 10^4 \text{ rad/s} \\ \omega_2 &\approx 4.5 \times 10^6 \text{ rad/s} \end{aligned} \right\} -3 \text{ dB points}$$

- (b) If $V_i(t) = 0.5 \cos(2000t)$ V, then what is $V_o(t)$ (again, reasonable estimates are okay)? [5 points]

$$-20 \text{ dB} = 20 \log_{10} \left(\frac{|V_o|}{|V_i|} \right) \text{ dB}$$

$$-1 = \log_{10} \left(\frac{|V_o|}{0.5} \right)$$

$$|V_o| = 0.05$$

$$\phi|_{\omega=2000 \text{ rad/s}} \approx 85^\circ$$

$$V_o(t) = 0.05 \cos(2000t + 85^\circ) \text{ V}$$

Continue on next page...

- (c) Solve for the values of R & L needed to achieve this transfer function, assuming that $C = 5.55$ nF and the quality factor for this circuit can be expressed as $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$. [10 points]

$$\omega_n = 3 \times 10^5 \text{ rad/s} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{L \times (5.55 \times 10^{-9} \text{ F})}} \rightarrow \boxed{L = 2 \text{ mH}}$$

$$Q = \frac{\omega_n}{B} = \frac{\omega_n}{\omega_2 - \omega_1} = \frac{3 \times 10^5}{(4.5 \times 10^6 - 2 \times 10^4)} = 0.067$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = 0.067 = \frac{1}{R} \sqrt{\frac{2 \times 10^{-3}}{5.55 \times 10^{-9}}}$$

$$\boxed{R \approx 9 \text{ k}\Omega}$$

03/23/09
09:39:38

bpf/bpf.m

1

```
% BME153L.02 (Spring 2009)
% Test #2 BPF Transfer Function Interpretation
% Mark Palmeri (mark.palmeri@duke.edu)
% 2009-03-21
```

```
R = 9000;
C = 5.55e-9;
L = 2e-3;
```


```
w = logspace(3,8,10000);
```

```
H = (i*w*C*R)./(1+i*w*C*R+((i*w).^2)*L*C);
```

```
subplot(2,1,1);
h=semilogx(w,20*log10(abs(H)));
set(h,'LineWidth',1,'Color','k');
xlabel('\omega (rad/s)','FontSize',14)
ylabel('|H(j\omega)| (dB)','FontSize',14)
set(gca,'YTick',[-40 -20 -12 -6 -3 0])
set(gca,'FontSize',14);
grid on;
a=axis;
axis([a(1) a(2) -25 0]);
```

```
subplot(2,1,2);
h=semilogx(w,angle(H)*360/(2*pi));
set(h,'LineWidth',1,'Color','k');
xlabel('\omega (rad/s)','FontSize',14)
ylabel('Phase (deg)','FontSize',14)
set(gca,'YTick',[-90:45:90]);
grid on;
set(gca,'FontSize',14);
```

```
print -deps2 bpf.eps
```

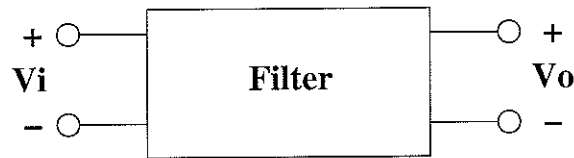Problem #2 [35 points] $\left(\frac{28.4}{35}\right)$ 

You are designing a filter for a signal coming out of an ultrasound scanner. The desired signal content ranges in frequency from 1-10 MHz, but there is significant noise ≤ 100 Hz. You must design a first-order filter that:

- Attenuates noise ≤ 100 Hz at least 40 dB below the desired signal content (1-10 MHz),
- Does not distort the phase of the desired signal content (1-10 MHz) more than 15° .

(a) What type of filter do you need? Why? [5 points]

HPF; need to preserve high f content while attenuating low f noise.
Can't use BPF b/c it is 2°.


(b) What is/are the cutoff frequency/frequencies of your filter? [5 points]

1° HPF attenuates -20 dB/decade below ω_c + phase distortion $\rightarrow 0 \sim 1$ decade above ω_c

$$\therefore f_c \left\{ \leq 1 \times 10^5 \text{ Hz} + \geq 1 \times 10^4 \text{ Hz} \rightarrow 5 \times 10^4 \text{ Hz} \right.$$

$$\omega_c = 2\pi(5 \times 10^4 \text{ Hz}) = 3.14 \times 10^5 \text{ rad/s}$$

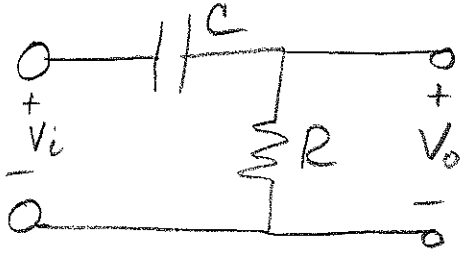- (c) Using 1 k Ω resistors and any value capacitors and/or inductors, draw a circuit diagram, including component values, for your filter that achieves the objectives described above. [5 points]



$$R = 1 \text{ k}\Omega$$

$$\omega_c = 3.14 \times 10^5 \text{ rad/s}$$

$$\omega_c = \frac{1}{RC} \rightarrow 3.14 \times 10^5 = \frac{1}{(1 \times 10^3)C}$$



$$C = 3.185 \text{ nF}$$

- (d) Derive (don't just state) the transfer function ($H(j\omega)$) for your filter. [5 points]

$$V_o(j\omega) = V_i(j\omega) \frac{R}{R + \frac{1}{j\omega C}}$$

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{j\omega RC}{1 + j\omega RC} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}} \angle \left[\frac{\pi}{2} - \tan^{-1}(\omega RC) \right]$$

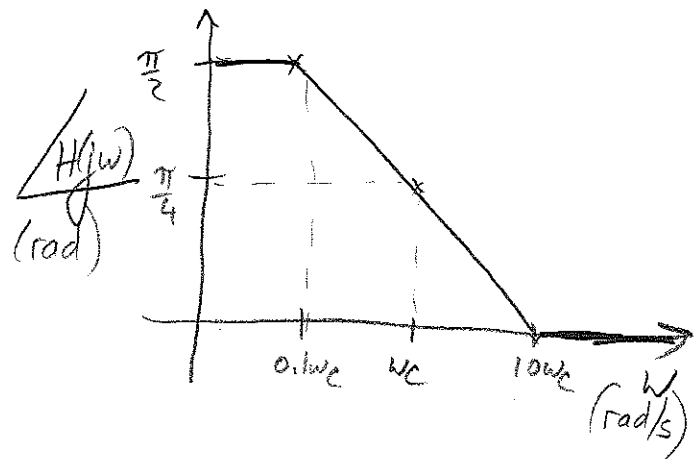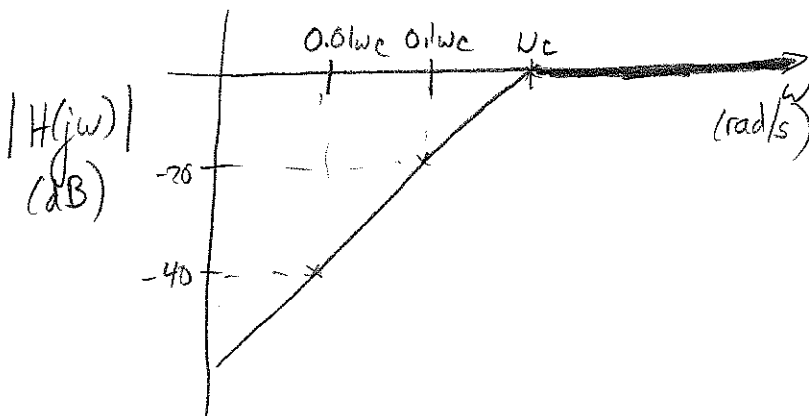- (e) Draw the Bode plot for your filter, including both magnitude and phase, labeling all important features and axes. [5 points]



Continue on the next page...

BME153L.02 - Test #2

Name: Answer Key



- (f) If your input signal is $V_i(t) = 100 \cos(2e6\pi t)$ V, then what is the filter's output ($V_o(t)$)? In addition to writing the expression for $V_o(t)$, plot $V_o(t)$ below the plot of $V_i(t)$. Remember to label the voltage axis. (Check yourself - this input signal should be in the passband of your filter - remember the stated filter objectives.) [5 points]

Using Bode plot or transfer function...

$$V_o(t) = 100 \cos(2e6\pi t + 2.9^\circ) \text{ V}$$

not attenuated ✓



$\angle 15^\circ$ ✓

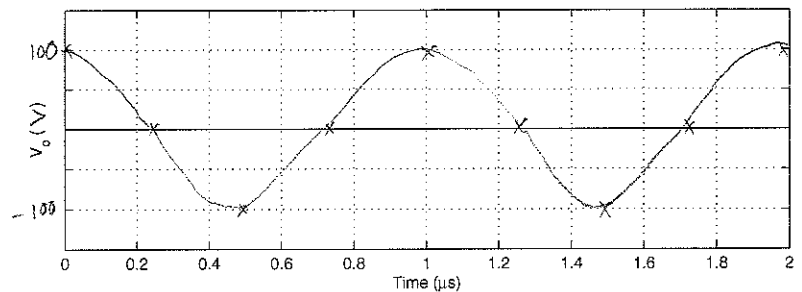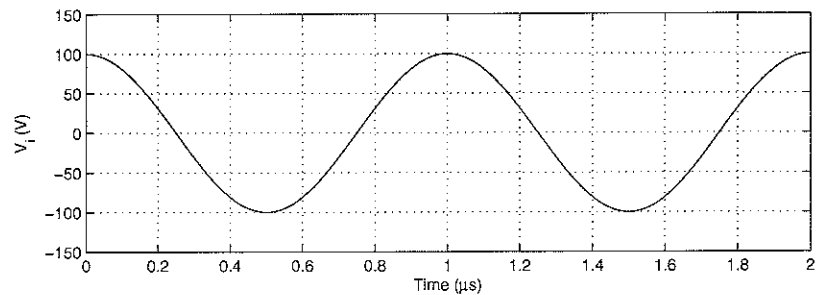


- (g) Repeat (f) for $V_i(t) = 100 \cos(200\pi t)$ V. (Check yourself - this input signal should be in the noise band - remember the stated filter objectives.) [5 points]

$$V_o(t) = 0.2 \cos(200\pi t + 90^\circ)$$

$\angle -49 \text{ dB}$ ✓

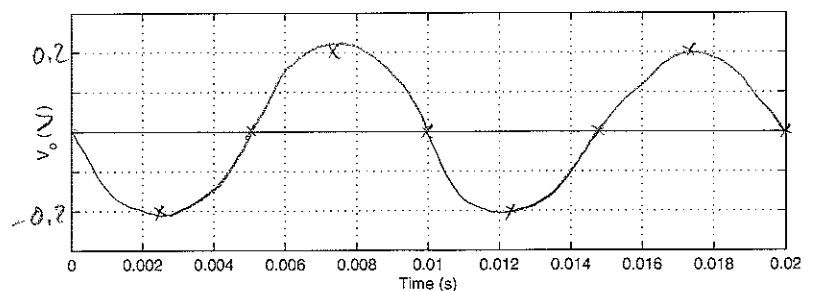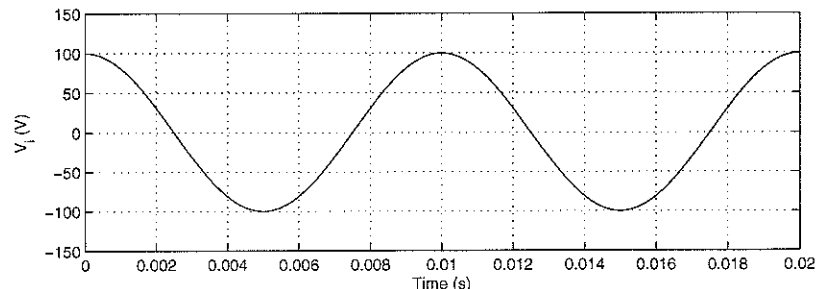

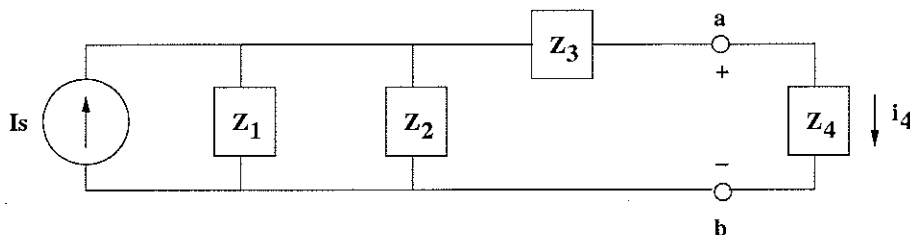Problem #3 [25 points] $\left(\frac{19.3}{25}\right)$ 

$$I_s(t) = 10 \cos(1000t) \text{ mA}$$

$$Z_1 = 20 \Omega$$

$$Z_2 = 30 \Omega$$

$$Z_3 = ?$$

$$Z_4 = \text{variable load}$$


$Z_{1..4}$ represent discrete components in the circuit (i.e., resistors, capacitors, and inductors). When $Z_4 = \infty$ (open circuit across terminals a & b), $v_{ab} = 120 \cos(1000t) \text{ mV}$, and when $Z_4 = 0$ (short circuit across terminals a to b), $i_4 = 9.86 \cos(1000t + 9.46^\circ) \text{ mA}$.

- (a) What is the Norton impedance for the circuit as seen from Z_4 (i.e., Z_4 acts as the load)? [5 points]

$$Z_n = \frac{V_{oc}}{i_{sc}} = \frac{120 \times 10^{-3}}{9.86 \times 10^{-3} \angle 9.46^\circ} = 12.17 \angle -9.46^\circ \Omega$$

$$= \boxed{12.0 - 2j \Omega}$$

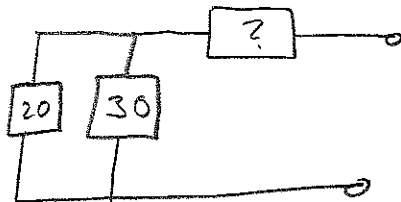- (b) Given Z_T , what is Z_3 ? [5 points]



$$12 - 2j = Z_3 + 12$$


$$\boxed{Z_3 = -2j \Omega}$$

- (c) Is Z_3 a resistor, a capacitor, or an inductor? What is the value of this component? [5 points]

Capacitor (-90° phase shift)

$$Z_3 = -2j = \frac{-j}{\omega C} \quad \omega = 1000 \text{ rad/s} \quad \rightarrow \quad \boxed{C = 500 \mu\text{F}}$$

Continue on the next page...

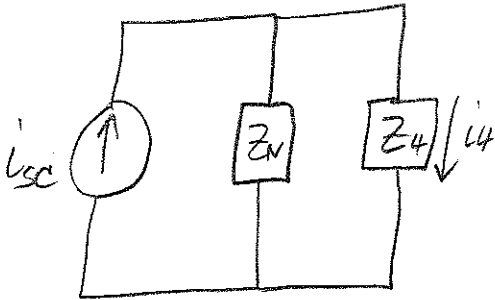(d) Solve for $i_4(t)$ if Z_4 is a 5 mH inductor. [5 points]

$$Z_4 = j\omega L = 5j \Omega$$

$$i_4 = 9.86 \angle 9.46^\circ \frac{12.17 \angle -9.46^\circ}{12 - 2j + 5j} \text{ mA}$$

$$i_4 = \frac{120}{12 - 2j + 5j} = \frac{120}{12 + 3j} = 9.7 \angle -14^\circ \text{ mA}$$


$$i_4(t) = 9.7 \cos(1000t - 14^\circ) \text{ mA}$$

(e) Solve for $v_{ab}(t)$ if Z_4 is a 5 mH inductor (same as (d)). [5 points]

$$v_{ab}(t) = v_4(t) = L \frac{di_4(t)}{dt} = (5 \times 10^{-3}) (-1000) (9.7) \sin(1000t - 14^\circ) \text{ V}$$

$$v_{ab}(t) = -48.5 \sin(1000t - 14^\circ) \text{ mV}$$

$$v_{ab}(t) = 48.5 \cos(1000t + 76^\circ) \text{ mV}$$

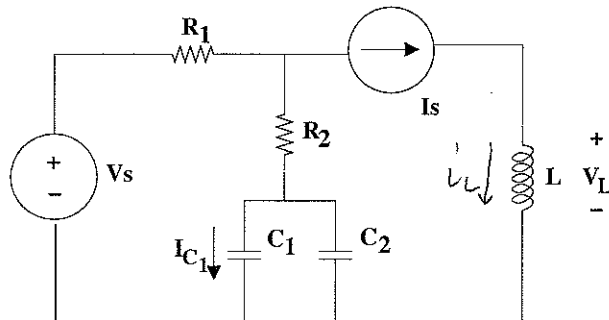Problem #4 ²⁰ ~~15~~ points] $\left(\frac{10.8}{20}\right)$


$$\begin{aligned}
 V_s(t) &= 20 \cos(100t) \text{ V} \\
 I_s(t) &= 10 \cos(1000t + 20^\circ) \text{ mA} \\
 R_1 &= 100 \Omega \\
 R_2 &= 500 \Omega \\
 C_1 &= 250 \mu\text{F} \\
 C_2 &= 750 \mu\text{F} \\
 L &= 5 \text{ mH}
 \end{aligned}$$

Assume that all of the sources have been on for a long time (i.e., the circuit is in a steady-state condition).

(a) Solve for an expression for $V_L(t)$. [5 points]


$$V_L = i_L Z_L = (10 \angle 20^\circ) (j 1000 \times 5 \times 10^{-3}) = 50 \angle 110^\circ$$

$$V_L(t) = 50 \cos(1000t + 110^\circ) \text{ mV}$$

(b) Solve for an expression for $I_{C_1}(t)$. [15 points]

$$C_{eq} = C_1 + C_2 = 1000 \mu\text{F}$$

Using superposition...

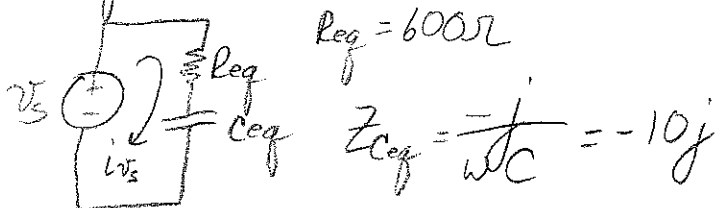


$$i_{V_s} = \frac{V_s}{Z_{eq} + Z_{Ceq}} = \frac{20 \angle 0}{600 - j10} = 0.0333 \angle 1.0^\circ$$

$$\text{Current Division w/ } C_{eq}: i_{C_1, V_s} = i_{V_s} \frac{Z_{C_1}}{Z_{C_1} + Z_{C_2}} = 0.0333 \angle 1.0^\circ \frac{-13.33j}{-40j - 13.33j}$$

$$i_{C_1, V_s}(t) = 0.0083 \cos(100t + 1.0^\circ) \text{ A}$$

Continue on the next page if necessary...

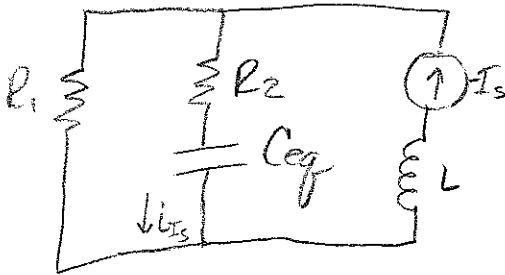Name: Answer Key

$$Z_{eq} = \frac{1}{j\omega C} = -j$$

$$i_{I_s} = -I_s \frac{100}{160 + 500 - 10j}$$

$$= -10 \angle 20^\circ \frac{100}{600 - j}$$

$$= \frac{-10 \angle 20^\circ}{600 \angle 0.1^\circ} (100) = -\frac{5}{3} \angle 19.9^\circ$$

$$i_{C_1 I_s} = i_{I_s} (0.25) = -\frac{5}{12} \angle 19.9^\circ$$

$$i_{C_1 I_s}(t) = \left(-\frac{5}{12} \angle 19.9^\circ \right) \cos(1000t + 19.9^\circ) A$$

$$i_{C_1}(t) = 8.3 \cos(1000t + 1.0^\circ) - 0.417 \cos(1000t + 19.9^\circ) mA$$